

# Spirit Level Reaction Time Tester

Hardware Design

Group 25

Ameya Thete

Gourav Saha

Ishita Jaiswal

Ishika Parihar

Pranav Ballaney


Saransh Gokhale


18th April 2021

# Table of Contents

High-Level Block Diagram	03
8284 Clock Generator	04
Intel 8086	05
System Bus of 8086 (Address and Data)	06
System Bus of 8086 (Control)	07
Memory Interfacing	08
I/O Interfacing	09
7447 BCD-to-seven-segment Decoder	10
8255 Programmable Peripheral Interface	11
8254 Programmable Interval Timer	12
8259 Programmable Interrupt Controller	13
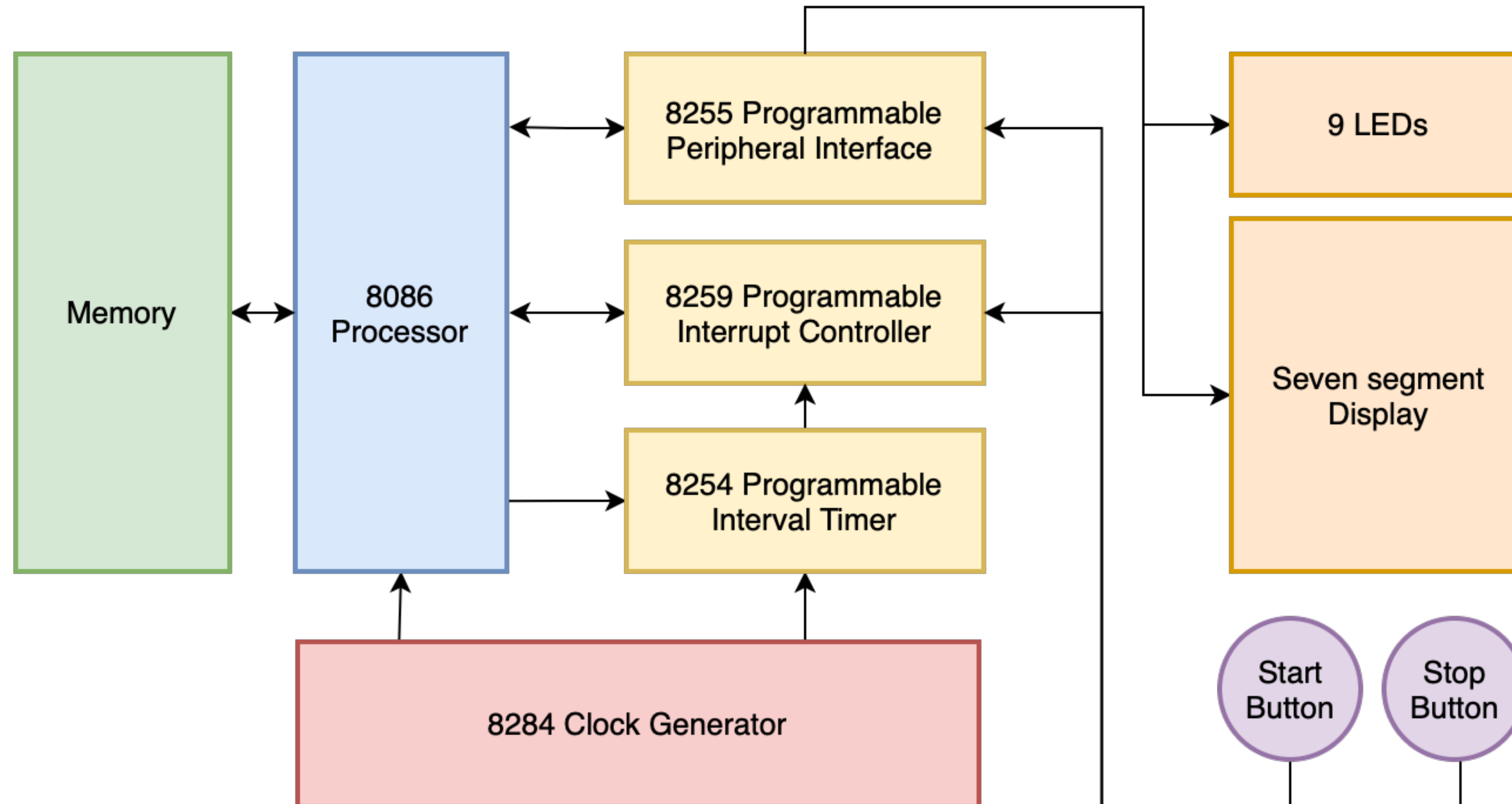
## A High-Level Block Diagram for the system




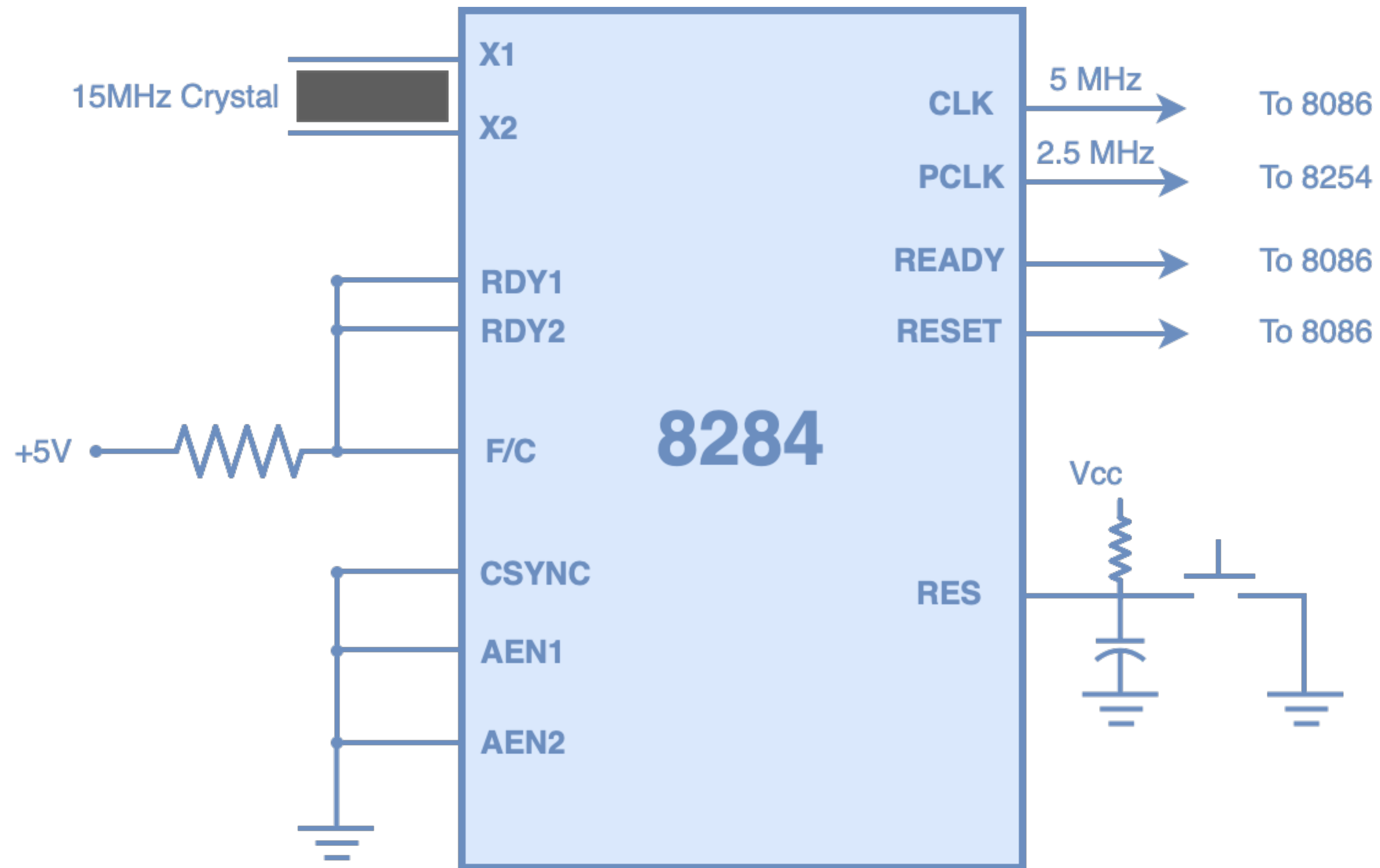


**8284 Clock Generator**

**Signals Generated**


- CLK at 5MHz
- PCLK at 2.5 MHz
- RESET
- READY

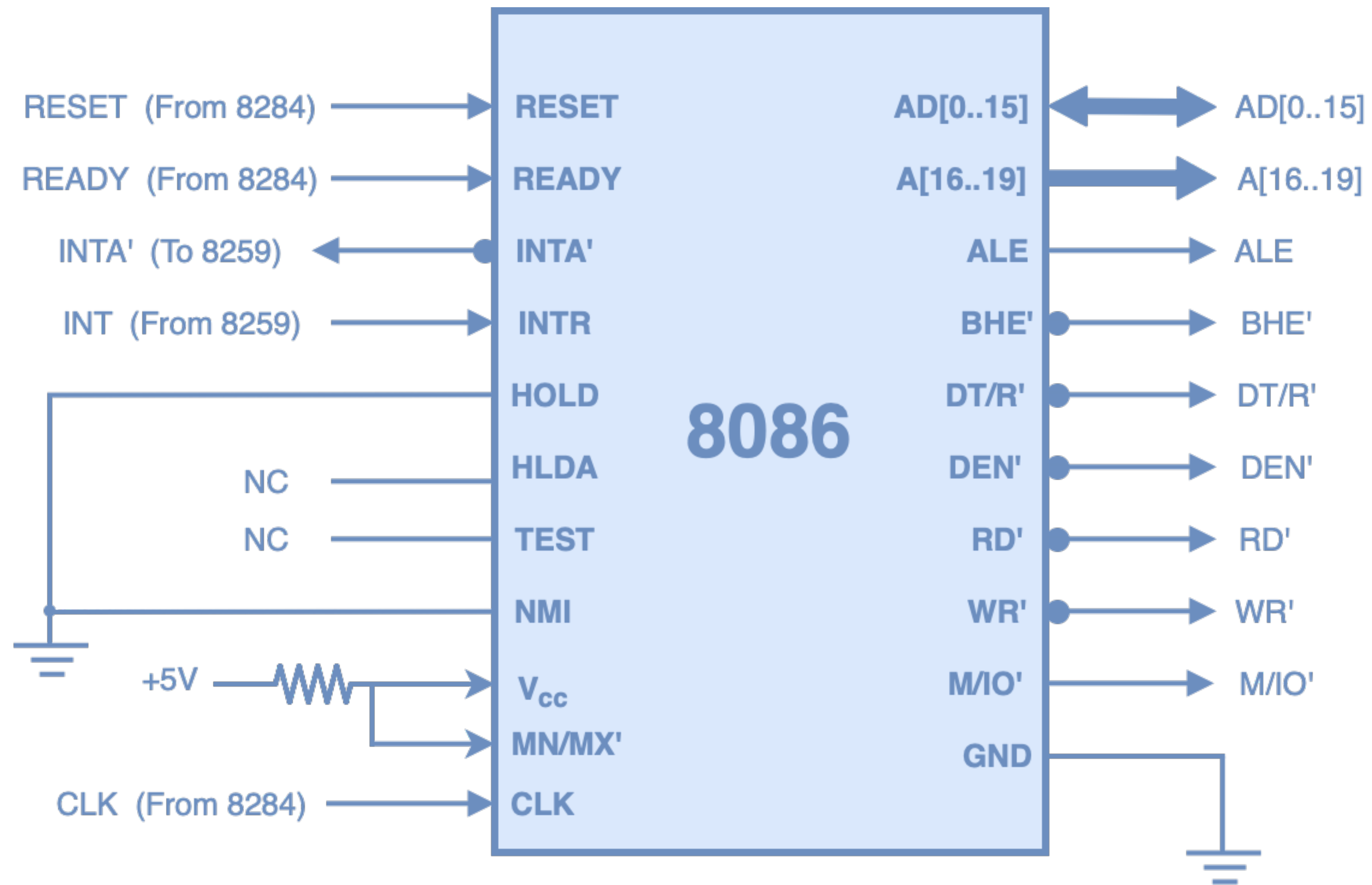

Intel 8086

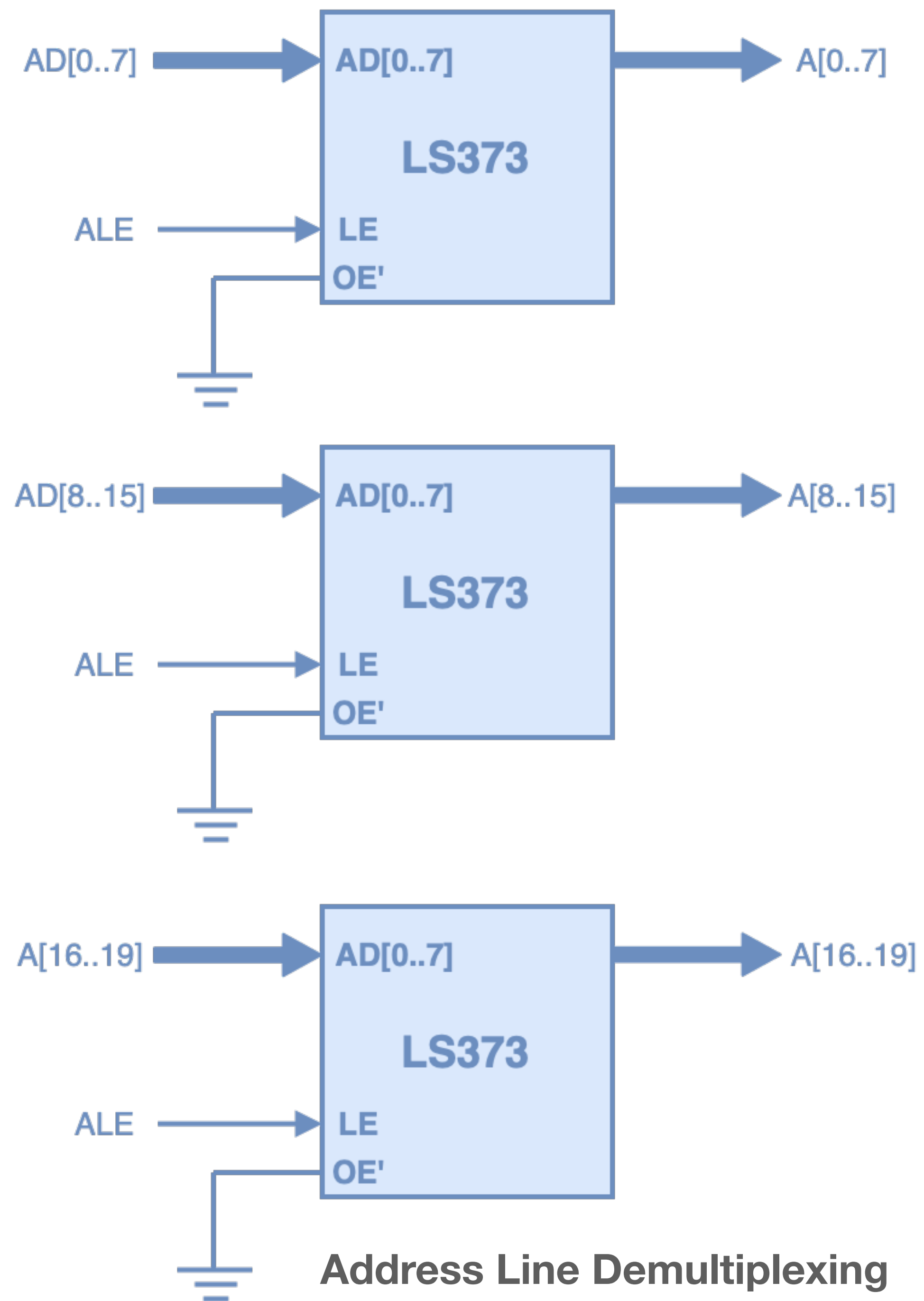


## System Bus of 8086 (Address and Data)

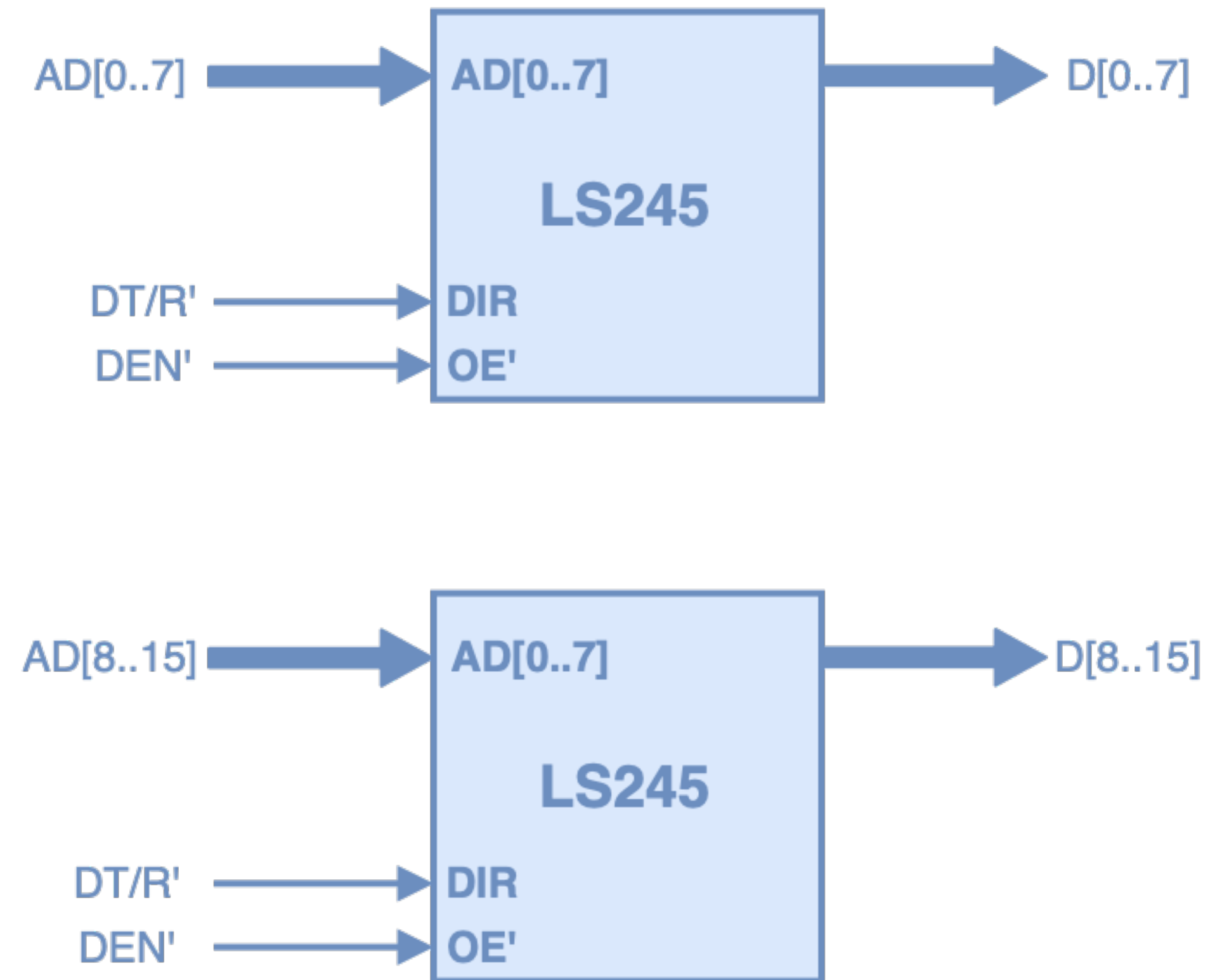


**Data Line Demultiplexing**

## System Bus of 8086 (Control)



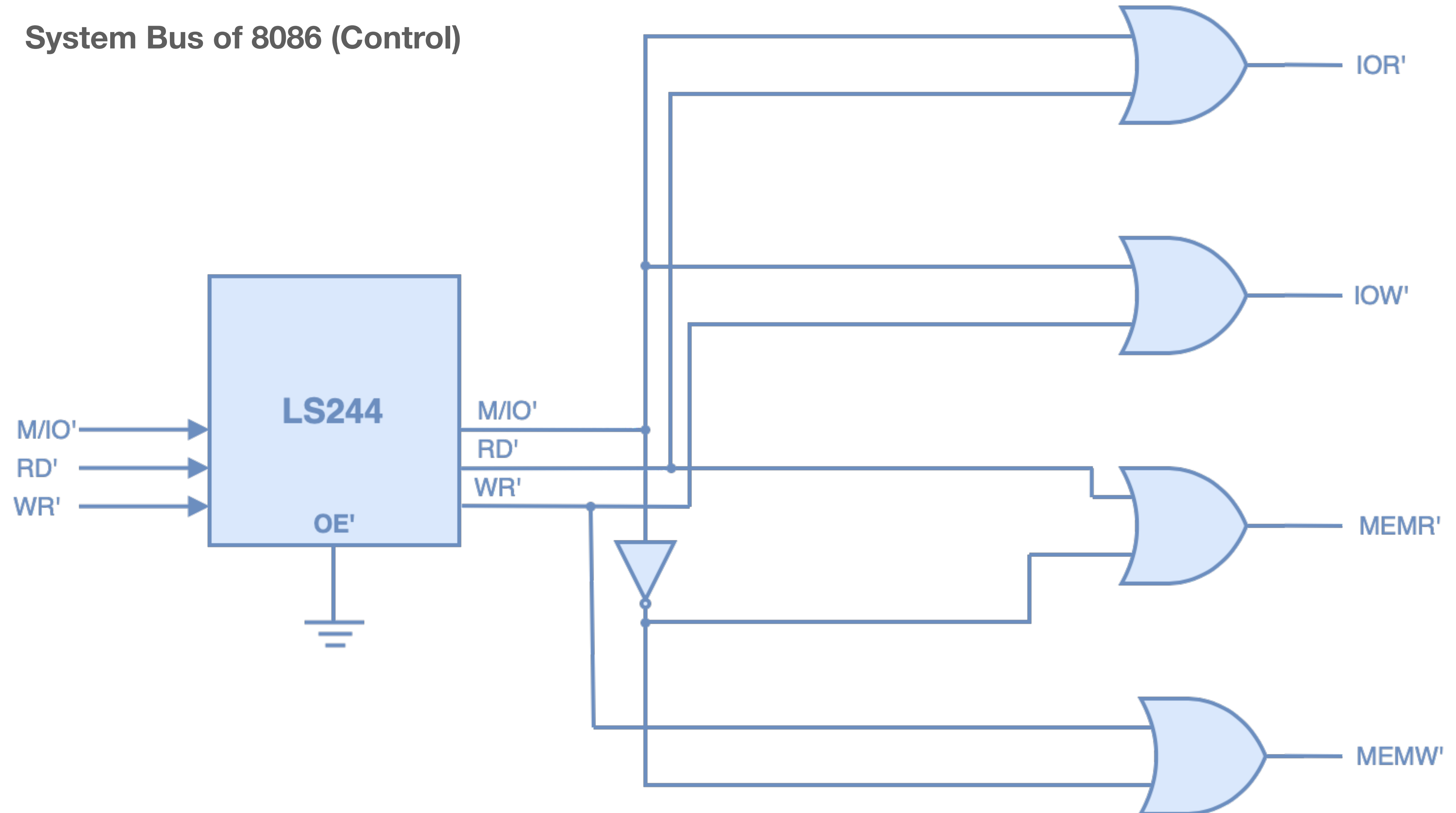


## Control Signal Generation

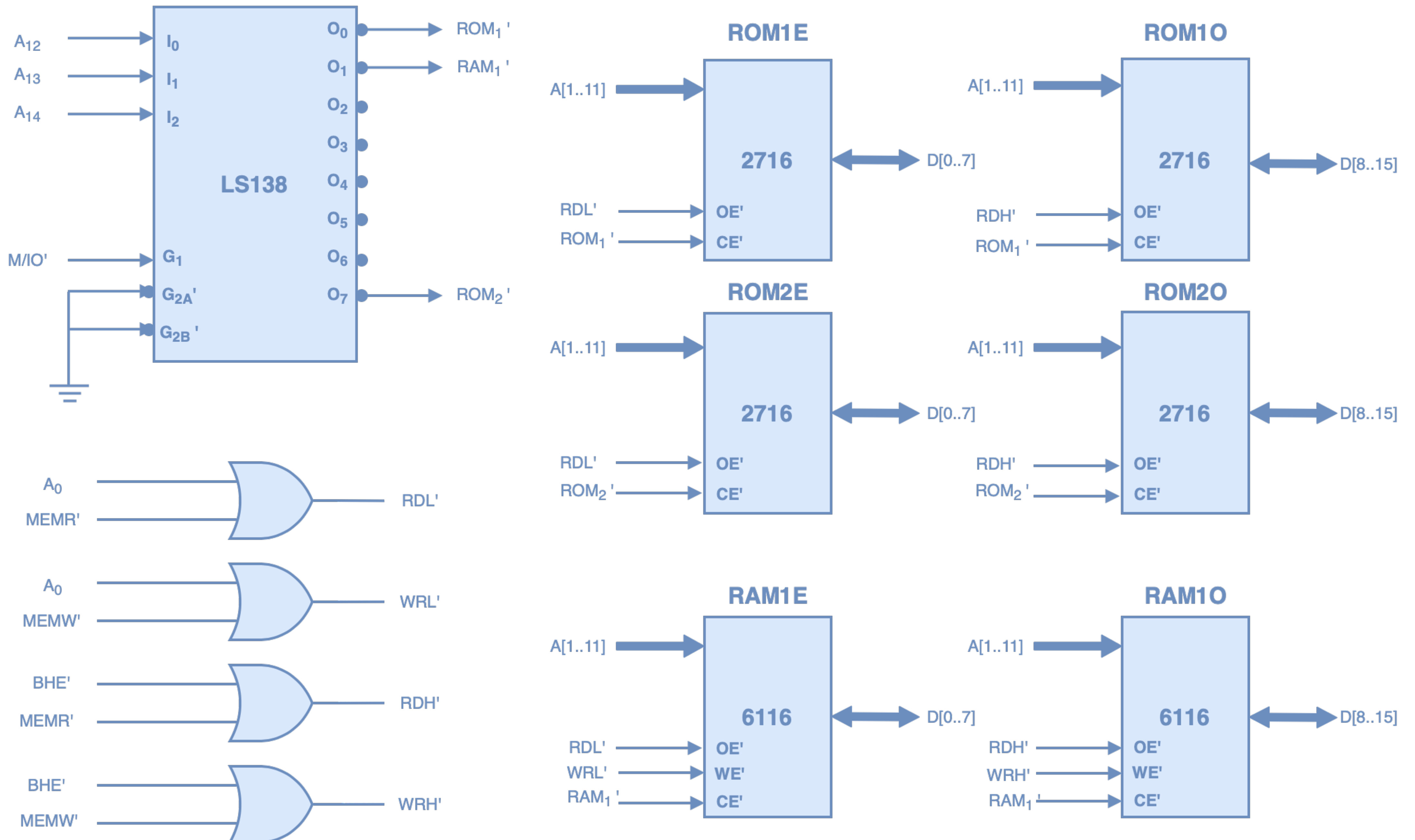


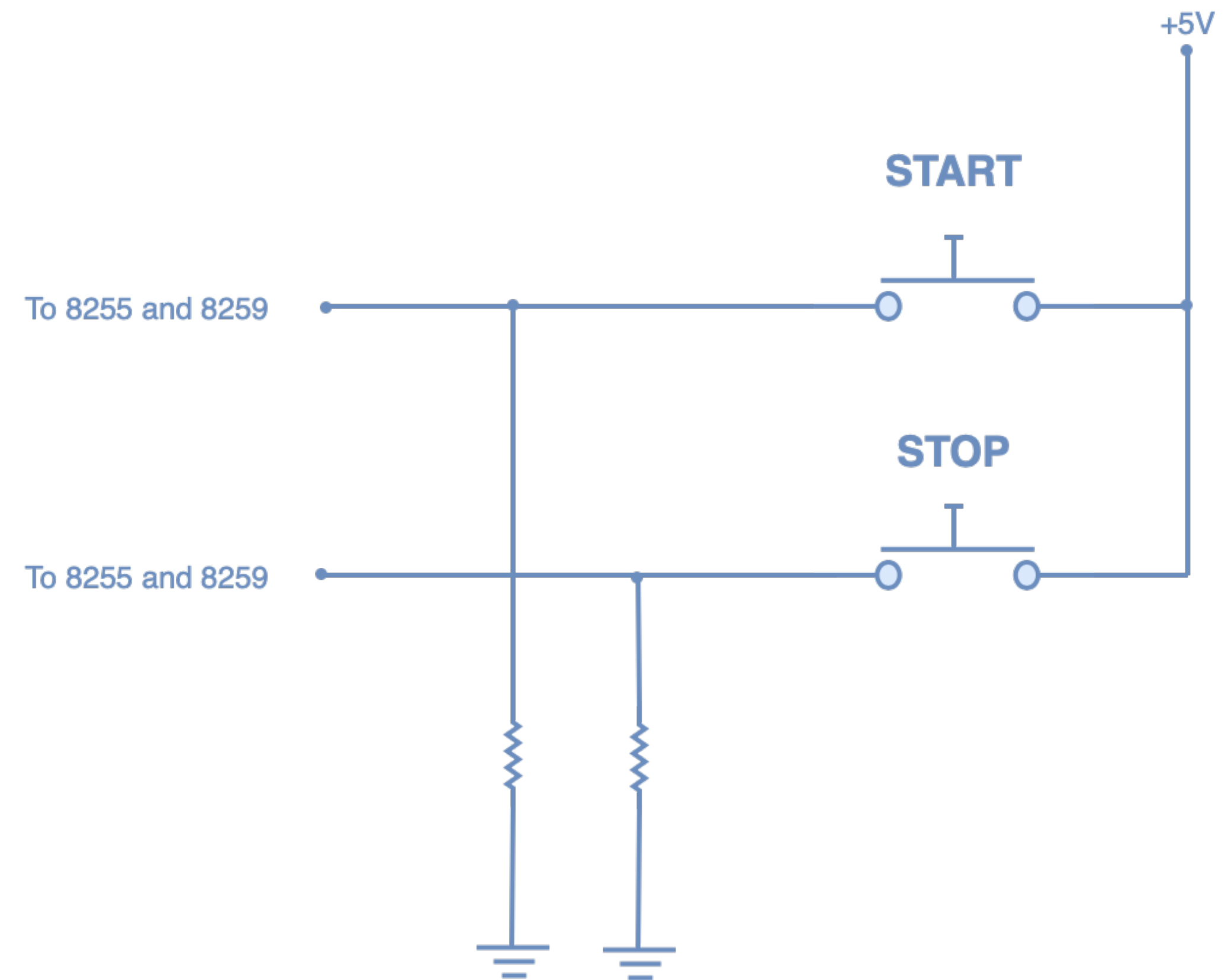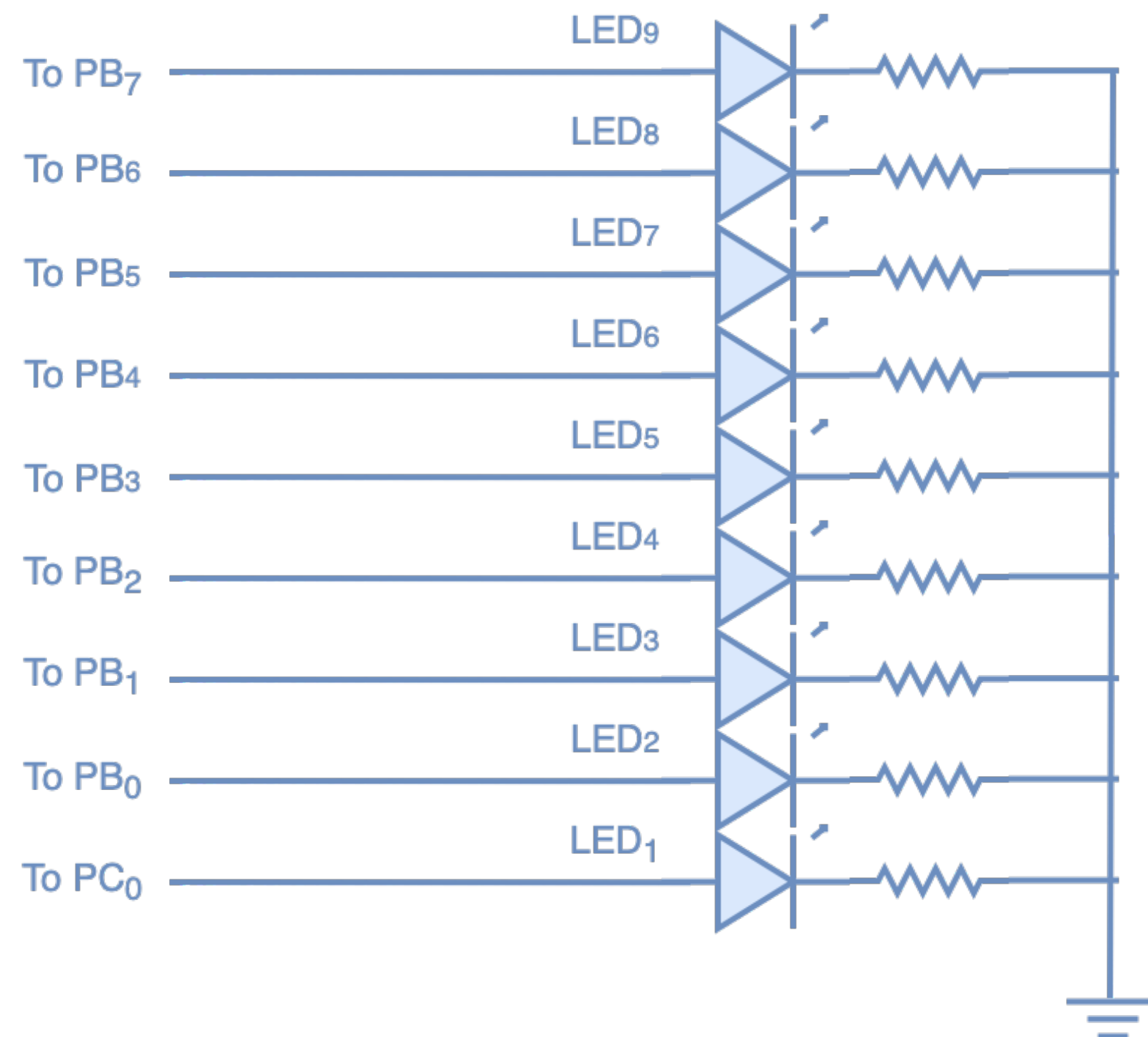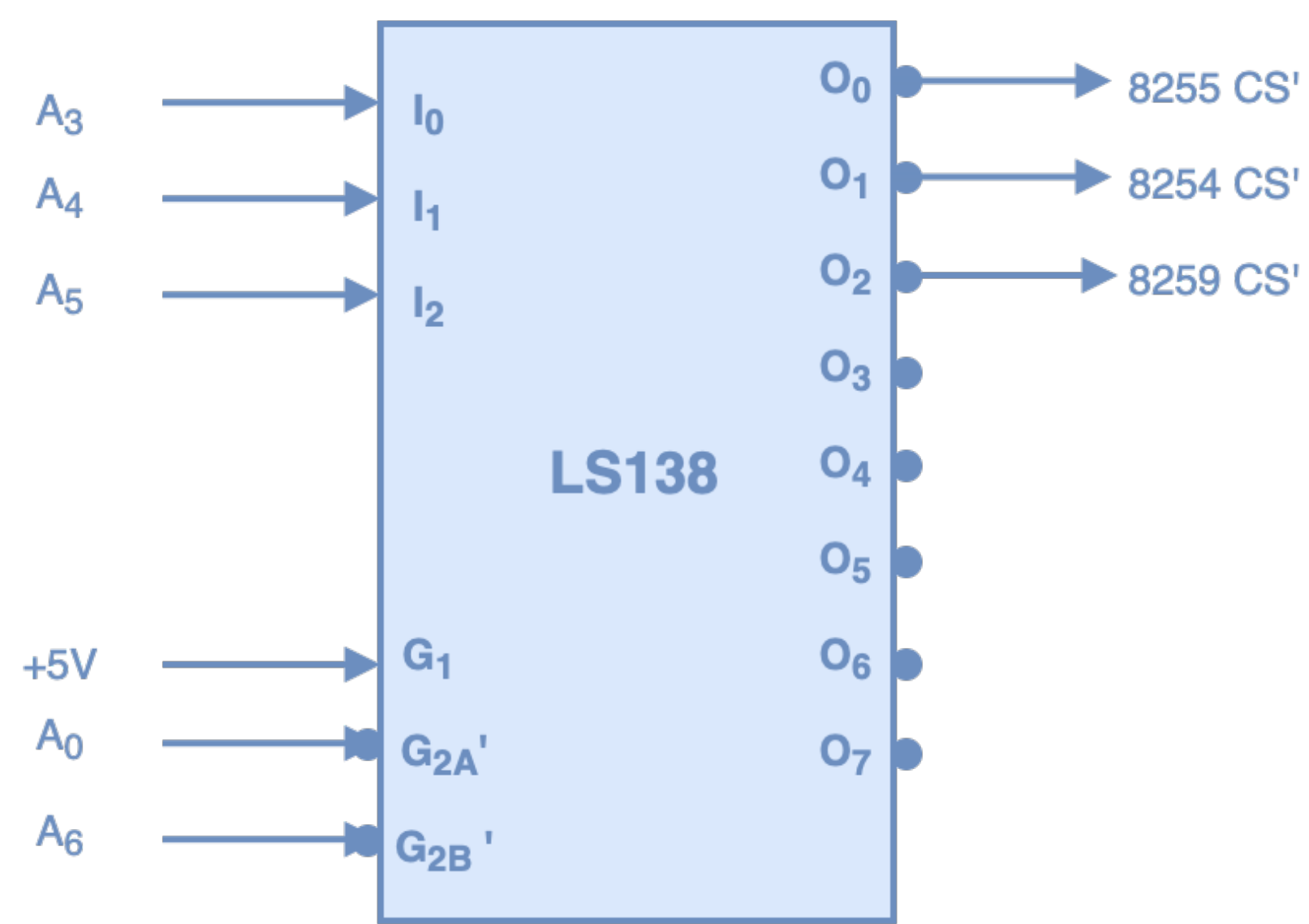Memory Decoder and Memory Chip Connections






## I/O Decoder and I/O Devices

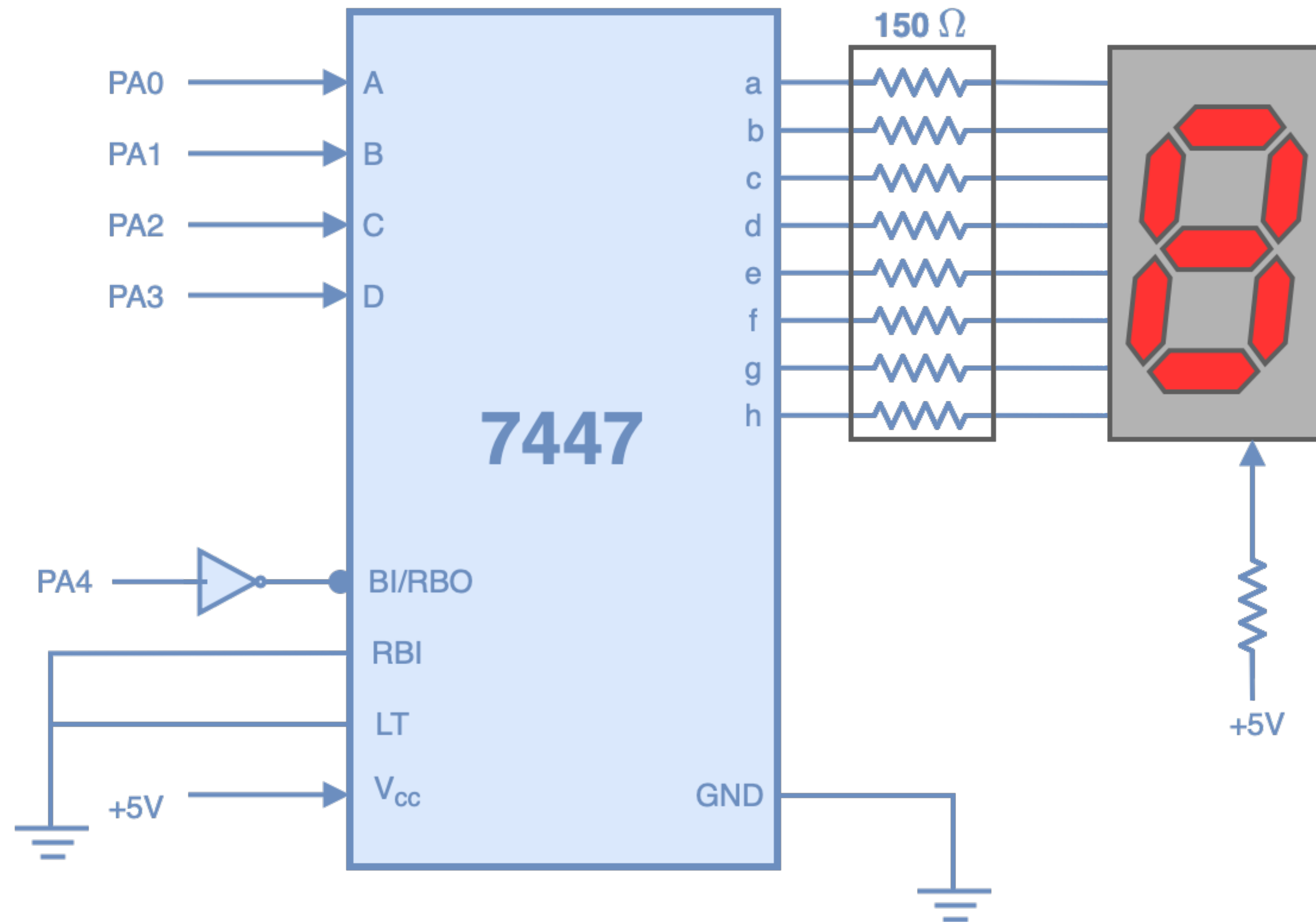

BCD-to-seven-segment Decoder Connections

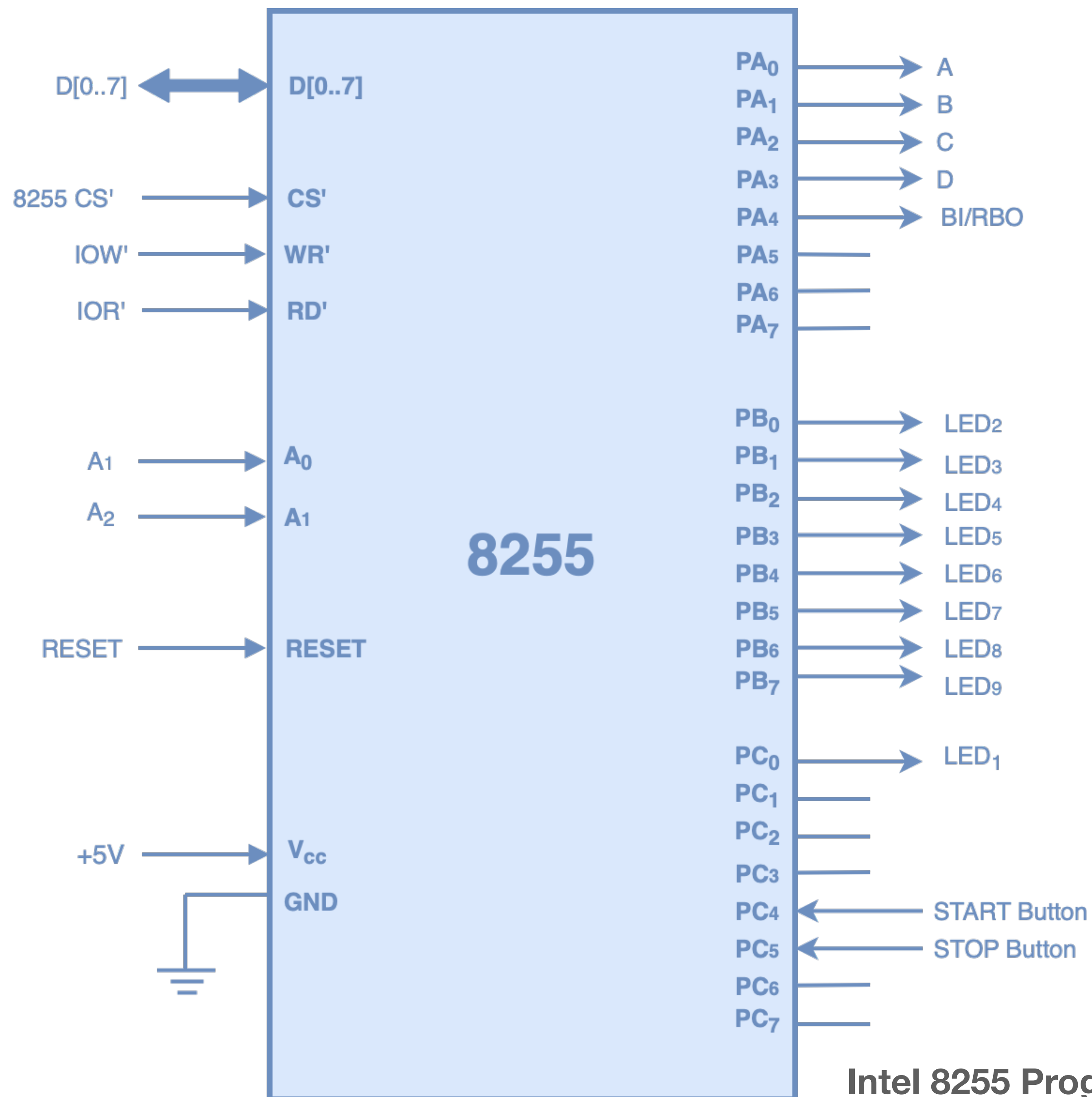


### Addresses

- Port A: 00h
- Port B: 02h
- Port C: 04h
- Control Register: 06h
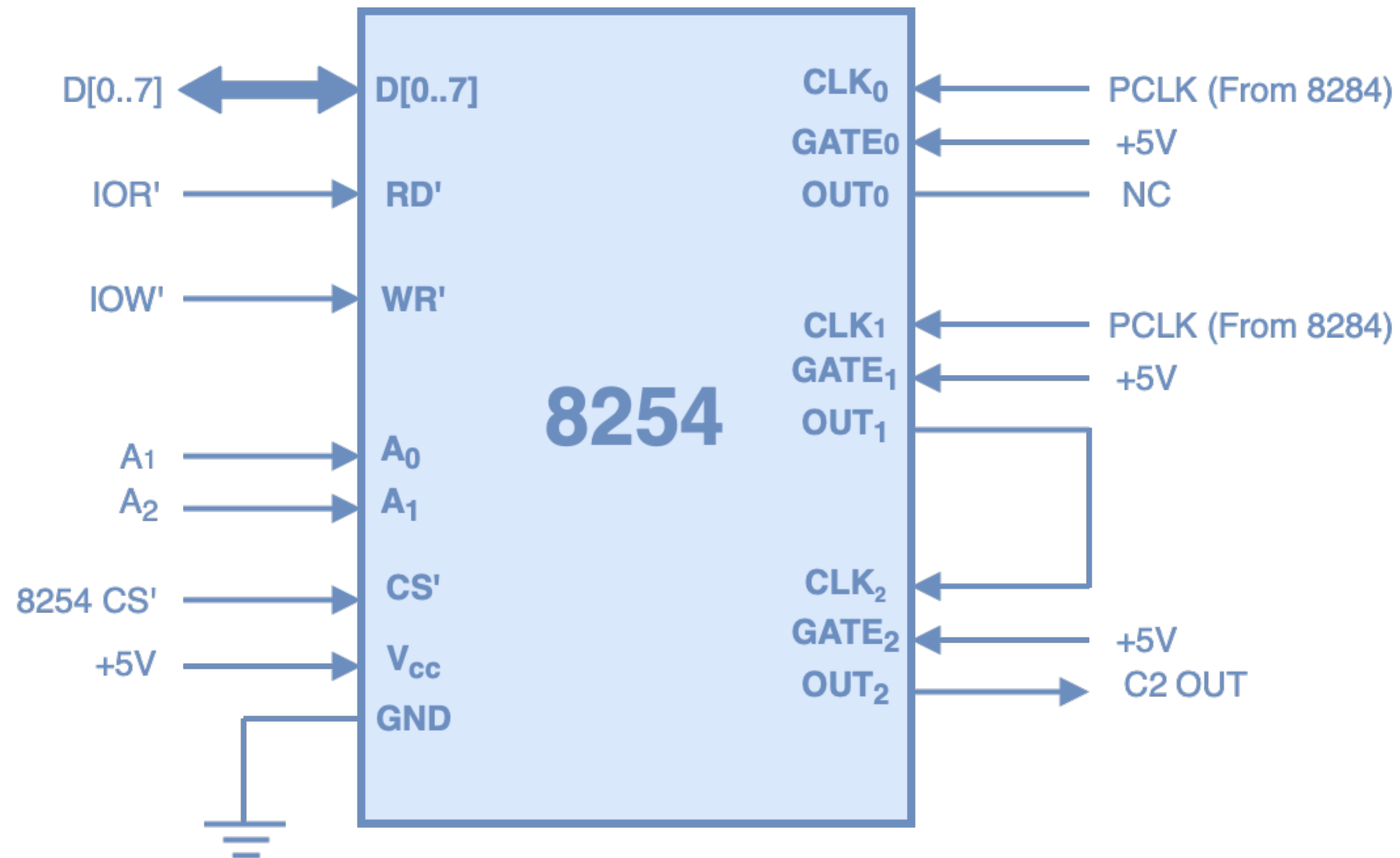
### I/O Devices Connected

- Port A (Output)
  - PA<sub>0</sub> - PA<sub>3</sub>: BCD inputs of IC 7447
  - PA<sub>4</sub>: BI/RBO of IC 7447
- Port B (Output): LED<sub>2</sub> - LED<sub>9</sub>
- Port C (Upper: Input, Lower: Output)
  - PC<sub>0</sub>: LED<sub>1</sub>
  - PC<sub>4</sub>: START button
  - PC<sub>5</sub>: STOP button



**Intel 8254 Programmable Interval Timer**

### Addresses


- Counter 0: 08h
- Counter 1: 0Ah
- Counter 2: 0Ch
- Control Register: 0Eh

### Configuration

- Counter 0: Mode 2 (Value: 161d)
- Counter 1: Mode 2 (Value: 62500d)
- Counter 2: Mode 2
  1. Value: 159d + readout from C0 (Random delay)
  2. Value: 2d for 50ms interrupt
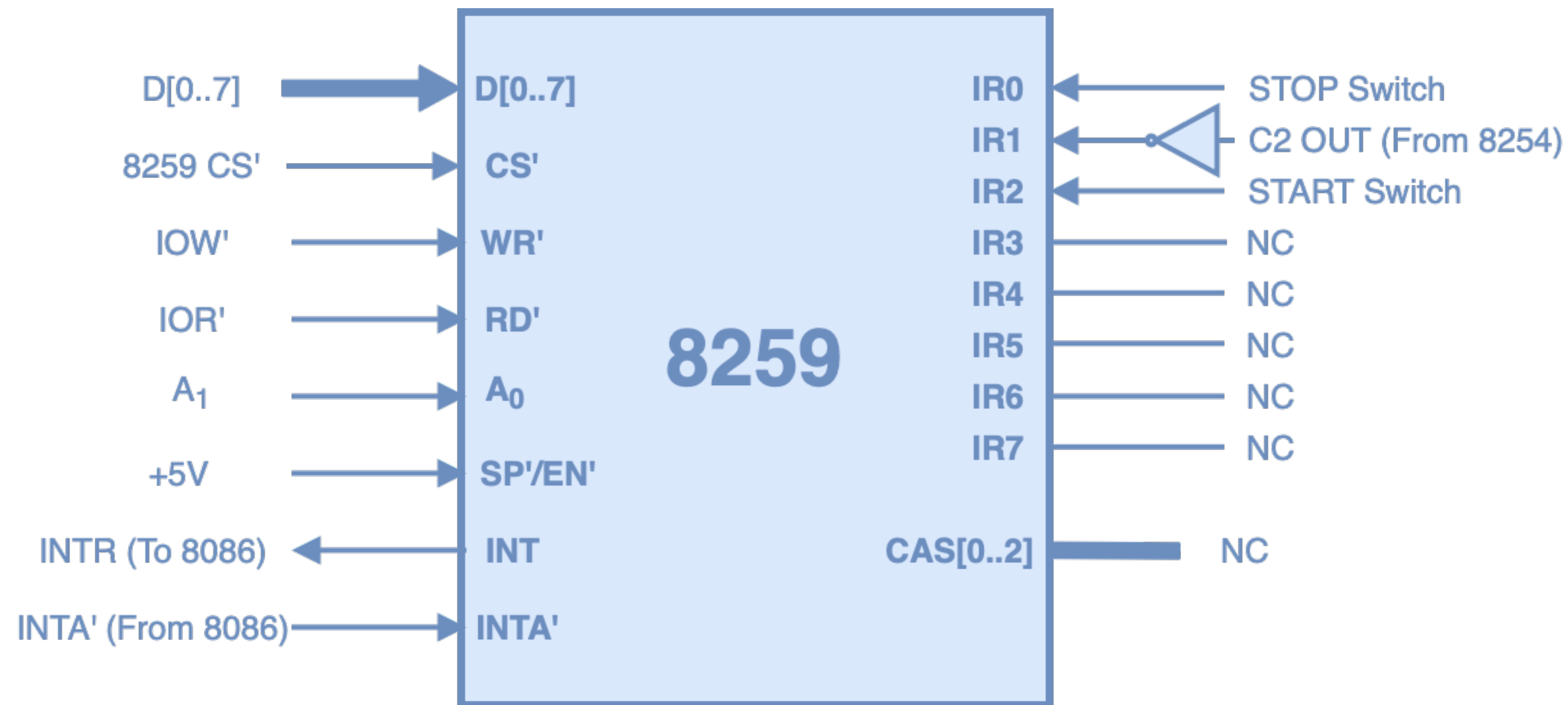
### Outputs

- OUT<sub>0</sub> not used
- OUT<sub>1</sub> at 40 Hz
- OUT<sub>2</sub> at
  1. 0.25Hz - 0.125Hz (random delay)
  2. 20 Hz (for lighting every successive LED)



**Intel 8259 Programmable Interrupt Controller**

### Inputs

- IR0: STOP Switch
- IR1: C2 OUT (OUT from counter 2)
- IR2: START Switch

### Addresses

10h - 12h